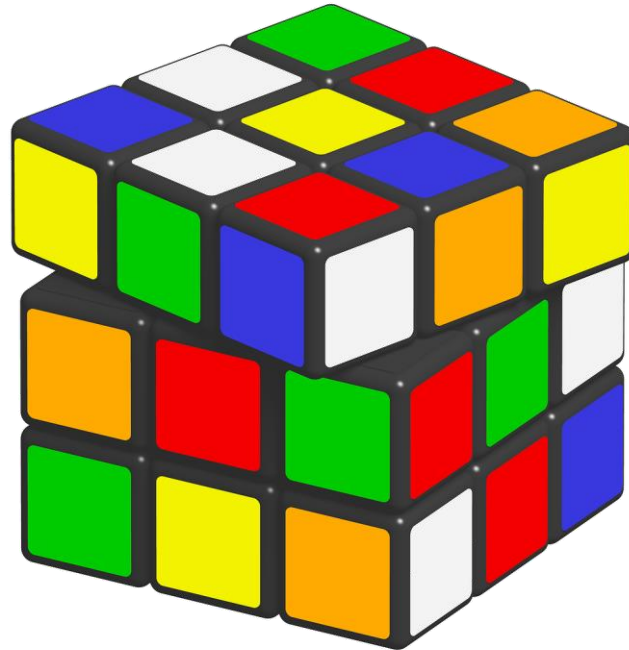



Architecture and CAD for FPGAs – ACF

Exercise 1 – LUT input pin-swapping



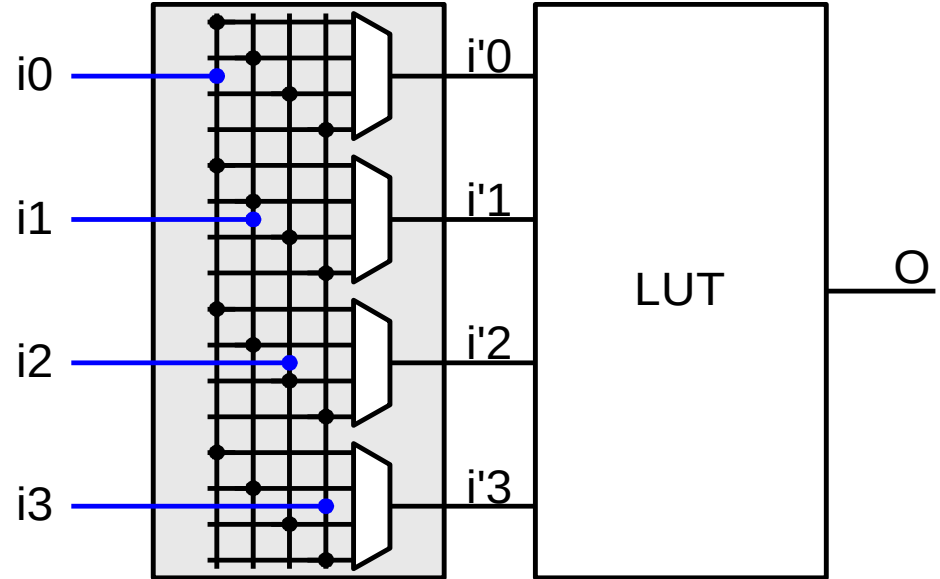Exercise – LUT input pin-swapping

- LUT pin-swapping implements a virtual input crossbar to the LUT
→ helps during routing
- Questions:
 - How does it work?
 - How do we permute the LUT entries?
 - Are there limits?
(situation where we cannot use this)
 - Are there other places where we can use this?



Look-up Tables – LUTs as function generators

[illegible]

Exercise – LUT input pin-swapping

- How do we permute the LUT entries?
- Swapping LUT inputs is just a permuting address bits to the LUT table
- We only have to copy bit-by-bit the table using the swapped address bit:

for i in 0000 to 1111 loop:

LUT(i_3' , i_2' , i_1' , i_0')' = LUT (i)




e.g., if we want to swap i_0 with i_1 , then

$i_0' = i_1$ and $i_1' = i_0$


- Can also be done by shifting
(e.g., when swapping only two inputs)

	A_3, A_2, A_1, A_0	LUT-value AND gate	LUT-value OR gate
1			
0	0000	0	0
1	0001	0	1
2	0010	0	1
3	0011	0	1
4	0100	0	1
5	0101	0	1
6	0110	0	1
7	0111	0	1
8	1000	0	1
9	1001	0	1
A	1010	0	1
B	1011	0	1
C	1100	0	1
D	1101	0	1
E	1110	0	1
F	1111	1	1

Exercise – LUT input pin-swapping

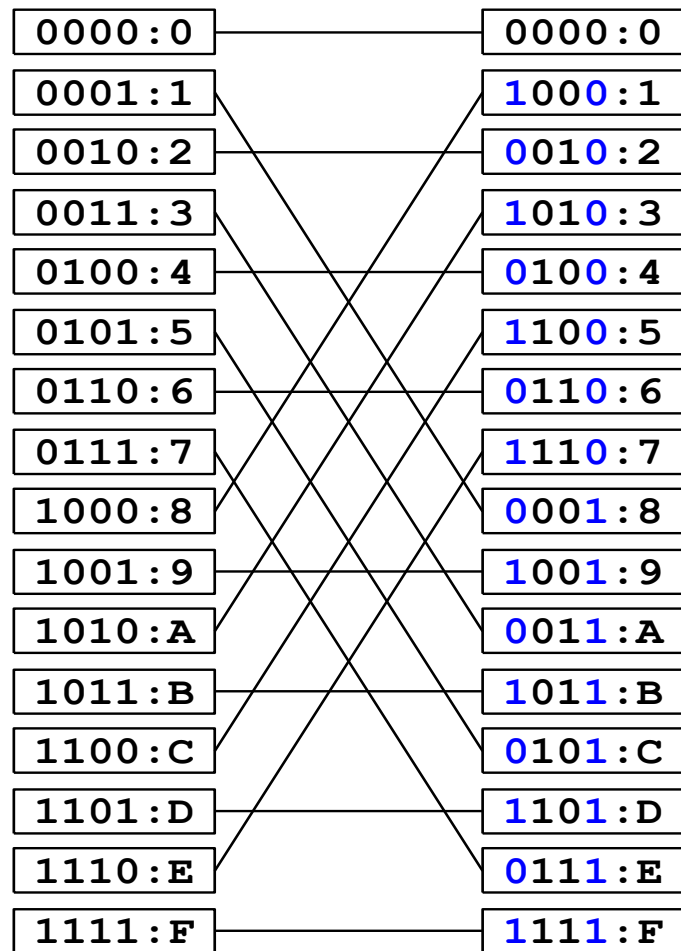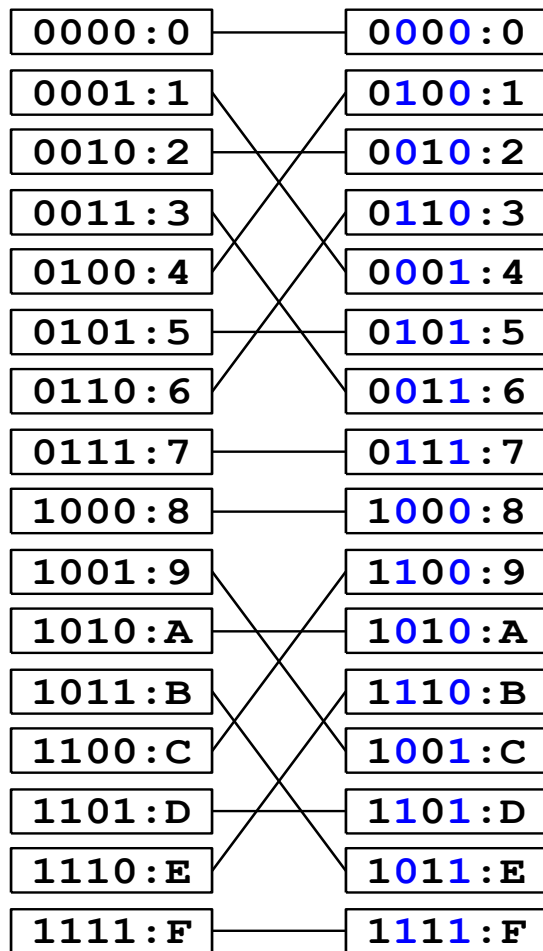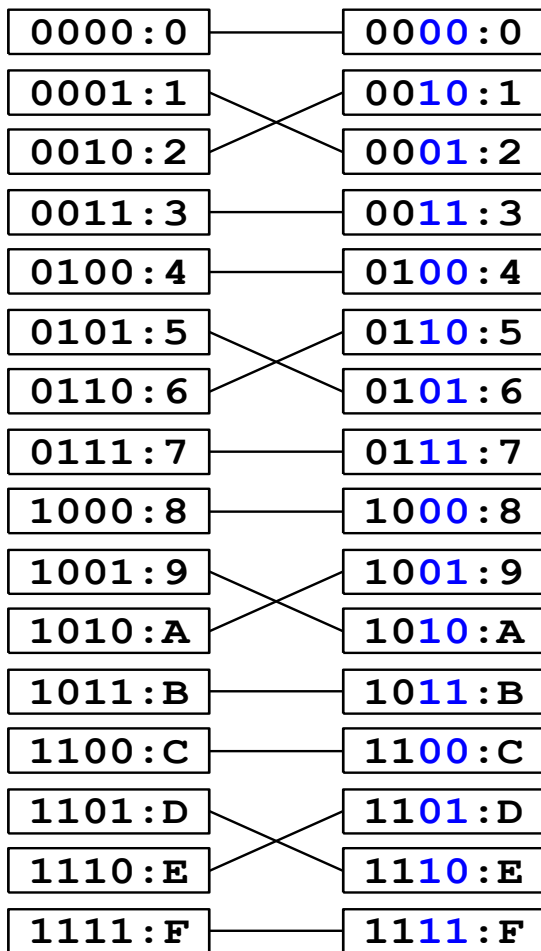

Exercise – LUT input pin-swapping

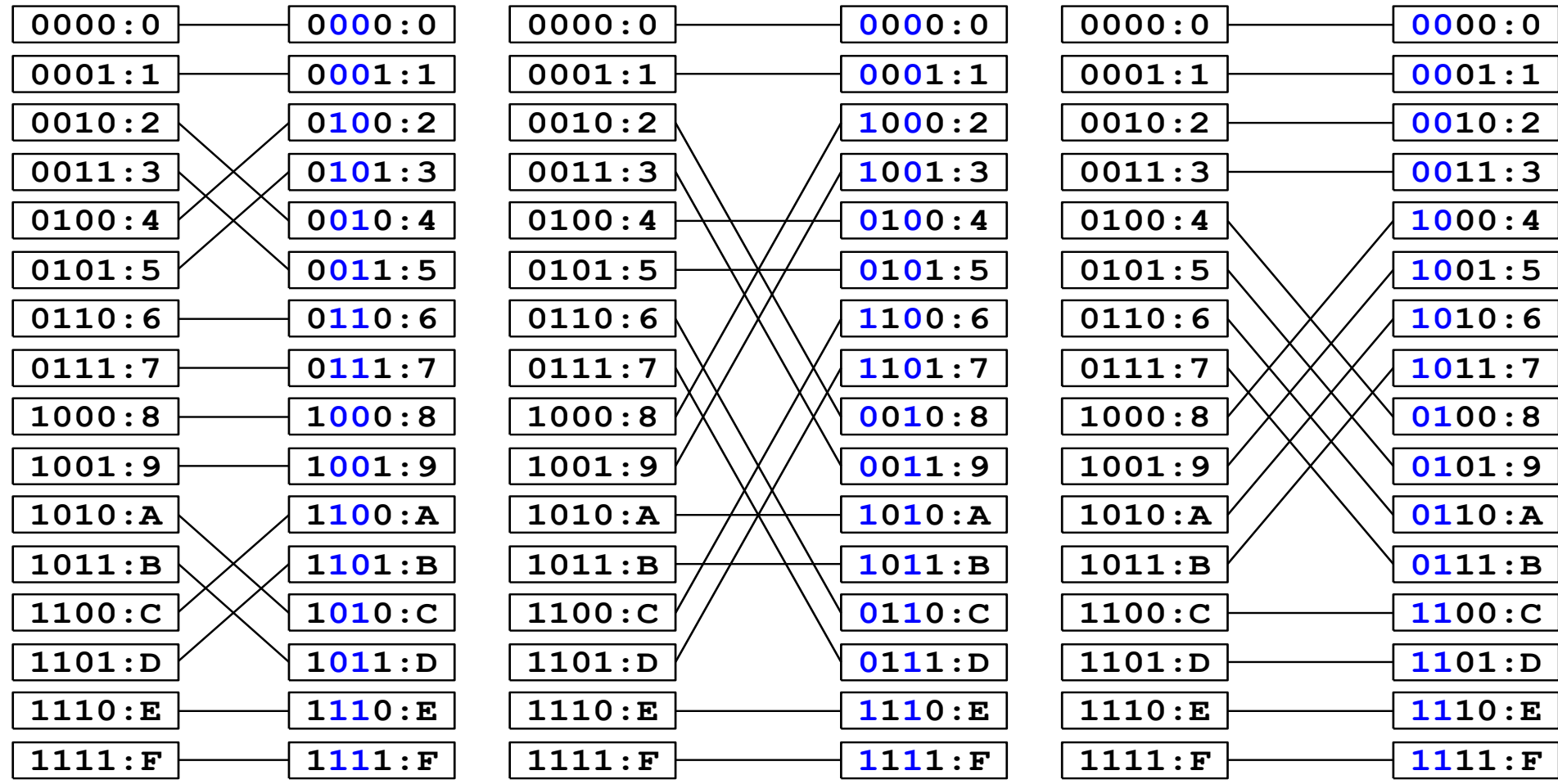

Exercise – LUT input pin-swapping

- Are there limits?
(situation where we cannot use this) 
- If the LUT is supporting distributed memory (like the shift-register or register-file mode), LUT inputs are addresses that cannot be swapped
- Are there other places where we can use this?
- BRAMs in ROM mode 
 - can be arbitrarily used for address and data bus (Xilinx does not do this) 
- Does not work in RAM mode
 - we usually use different read and write address ports and data is separated anyway (swapping creates a dependency with another port)

	A ₃ , A ₂ , A ₁ , A ₀	LUT-value AND gate	LUT-value OR gate
1			
0	0000	0	0
1	0001	0	1
2	0010	0	1
3	0011	0	1
4	0100	0	1
5	0101	0	1
6	0110	0	1
7	0111	0	1
8	1000	0	1
9	1001	0	1
A	1010	0	1
B	1011	0	1
C	1100	0	1
D	1101	0	1
E	1110	0	1
F	1111	1	1

Exercise – dependent LUT inputs

- **Write a function/program that gets in an init string and that returns the dependent variables.**

For instance, if someone has implemented a 3-input Boolean function in our LUT-4, you should detect which LUT input is unused

- For each bit index, we have to compare pairwise (by setting the bit index once 0 and once 1) if the LUT value is identical for all bit positions given by the index formed by the remaining bits (see figure)

# 0	0-+								0-+					0-+					0-+
#																			
# 1	0- -+									0- -+					0- -+				1-+
#																			
# 2	0- - -+									0- - -+					1-+				0-+
#																			
# 3	0- - - -+									0- - - -+					1-+-				1-+
#																			
# 4	0- - - - -+									1-+					0-+				0-+
#																			
# 5	0- - - - - -+									1----					0- -+				1-+
#																			
# 6	0- - - - - - -+									1-----					1-+				0-+
#																			
# 7	0- - - - - - - -+									1-----					1-+-				1-+
#																			
# 8	1-+									0-+					0-+				0-+
#																			
# 9	1----									0- -+					0- -+				1-+
#																			
# A	1-----									0- - -+					1-+				0-+
#																			
# B	1-----									0- - - -+					1-+-				1-+
#																			
# C	1-----									1-+					0-+				0-+
#																			
# D	1-----									1----					0- -+				1-+
#																			
# E	1-----									1-----					1-+				0-+
#																			
# F	1-----									1-----					1-+-				1-+

Any Questions?

